

### LIST OF EXPERIMENTS - PAGE 1/2

1	Wheel of Fortune	41	Voltage Drop	81	Code Practice Unit
2	The Noisy Light	42	Voltage Regulator	82	Light/Sound Code Practice Unit
3	Electronic Candle	43	LED - A Special Diode	83	Strobe Light
4	Rain Detector	44	How a Transformer Works	84	Noisy Strobe Light
5	Earsplitter	45	A Chopper Circuit	85	CdS-controlled Oscillator
6	Pencil Lead Organ	46	An AC Simulator	86	Shot in the Dark II
7	The Electric Human	47	Electronic Buzzer	87	Does Money Talk?
8	The Electrosonic Human	48	Photometer	88	"Crystal Set" Radio
9	Electric Birthday Cake	49	Electronic Jigsaw Puzzle	89	"Funny" Transistor Radio
10	Quick Draw	50	Night Light	90	One Transistor Radio
11	Quick Draw II	51	The Light Switch	91	Spark Gap Transmitter
12	Electronic Safecracking	52	Electronic Elephant	92	Morse Code Transmitter
13	UFO Invasion	53	Capital Letter Displays	93	Remote Water Level Detector
14	Tug of War	54	Small Letter Displays	94	AM Broadcaster
15	Shot in the Dark	55	Numeric Displays	95	Basic Audio Oscillator
16	Burglar Alarm	56	Meet the Transistor	96	Light-Controlled Bird
17	SOS Alert	57	Transistors as Switches	97	Electronic Motorcycle
18	Target Range	58	Electricity from Sound	98	Chirping Bird
19	"Catch" the Eight	59	Electric Money	99	Electronic Siren
20	Marching LEDs	60	A Push-Pull Amplifier	100	Fish Caller
21	Turn Signal Flasher	61	Understanding Oscillators	101	Plant Growth Stimulator
22	Leapin' LEDs!	62	A Push-Pull Oscillators	102	Electronic Organ
23	Lights Out	63	An Inverter Circuit	103	Electronic Raindrops
24	Light Telegraph	64	Meet the OR Circuit	104	Electronic Cat
25	Frontier Telegraph	65	Introducing the AND Gate	105	Electronic Bird
26	Introducing the Resistor	66	Using the NOR Gate	106	Digital Rhythm
27	Parallel Resistors	67	Meet the NAND Gate	107	Sound Machine I
28	Secret Resistance	68	How a Multivibrator Works	108	Sound Machine II
29	A Variable Resistor	69	A "One Shot" Multivibrator	109	Sound Machine III
30	Capacitors in Series and Parallel	70	An R-S Flip-flop	110	Electronic Coin Toss
31	The Electronic Gas Tank	71	Sound Scooper	111	Electronic Coin Toss II
32	Discharge Timer	72	Liquid Conductivity Tester	112	Even or Odd
33	Light Dimmer	73	Super-Sensitive Photometer	113	Electronic Roulette
34	The Quick Capacitor	74	Motion Detector	114	Electronic Dice
35	Electronic Timer	75	Two-Tone Buzzer	115	Roulette with Sound
36	Capacitors and Oscillators	76	Variable Capacitor Oscillator	116	The Light Fantastic
37	A Variable Capacitor	77	Variable RC Oscillator	117	ESP Tester
38	Resistors and Capacitors Together	78	Electronic Metronome	118	Close-In
39	Resistors and Capacitors Together II	79	Door Alarm	119	Three-Input OR Circuit
40	Meet the Diode	80	Frequency Shift Oscillator	120	Three-Input AND Circuit

### LIST OF EXPERIMENTS - PAGE 2/2

121	RTL Inverter	151	Shift Register	181	Crossing Signal
122	RTL Buffer	152	Basic Counter Circuit	182	Digital Timer
123	RTL OR Gate	153	Synchronous Counter	183	Set/Reset Buzzer I
124	RTL AND Gate	154	Asynchronous Counter	184	Set/Reset Buzzer II
125	DTL OR Gate	155	Counter with Line Decoder	185	Set/Reset Buzzer III
126	DTL AND Gate	156	Divide by 4 Counter	186	Optical Counter
127	DTL NOR Gate	157	Divide by 4 Counter with Line Decoder	187	LED Sound Meter
128	DTL NAND Gate	158	How a Line Decoder Works	188	Shot in the Dark III
129	DTL Exclusive OR Gate	159	Multiple Counter	189	Set/Reset Match
130	TTL Inverter	160	Binary Counter with Display	190	Number Displays
131	TTL Buffer	161	Divide by 3 Counter with Display	191	Circuit Continuity Checker
132	TTL OR Gate	162	Divide by 4 Counter with Display	192	Acoustic Ohmmeter
133	TTL AND Gate	163	Light or Sound	193	DC Voltmeter
134	TTL 3-Input AND Gate	164	Be Your Own Multivibrator	194	Voltage Level Detector
135	TTL NOR Gate	165	Anticipation	195	AC Voltmeter
136	TTL XOR Gate	166	Big Mouth!	196	Audio Signal Generator
137	TTL NAND Enable Circuit	167	Sound Stop	197	Volume Level Meter
138	TTL AND Enable Circuit	168	Multivibrator Switching	198	Capacitance Checker
139	TTL OR Enable Circuit	169	Winking LEDs	199	Diode Tester
140	TTL Line Selector	170	A Phony Counter?	200	Transistor Checker
141	TTL Data Selector	171	Alphabet Flasher		
142	TTL R-S Flip-flop	172	A One-Shot TTL		
143	TTL R-S Flip-flop II	173	Winking LEDs II		
144	Transistorized Toggle Flip-flop	174	Transistor Timer		
145	NAND Toggle Flip-flop	175	TTL Tone Generator		
146	J-K Toggle Flip-flop	176	Meet the VCO		
147	TTL Astable Multivibrator	177	Sound Out Timer		
148	TTL J-K Flip-flop	178	Buzzin' LED		
149	TTL D Flip-flop	179	Son of Buzzin' LED		
150	TTL Latch Circuit	180	Octave Generator		